## EEE270 Reactive Power Compensation (Power Factor Correction) Study Questions

Prepared by Prof. Dr. A. Mete VURAL

**Q1.** A single-phase 250 V (rms), 50 Hz supply feeds an inductive load drawing 13.46 A of current at a power factor of 0.73 lagging.

- **a**) Calculate the apparent power (S), real power (P), and reactive power (Q) consumed by the load.
- **b**) Determine the reactive power (Qc) that must be supplied by a capacitor connected in parallel with the load to improve the power factor to 0.95 lagging.
- c) Calculate the capacitance value (C) in microfarads (µF) required for the capacitor that provides the compensation found in part (b)
- d) Calculate the new total current drawn from the supply after power factor correction.
- e) Compare the original and improved conditions in terms of Power factor, Supply current, and Overall efficiency of power delivery

**Q2.** A 230 V (rms), 60 Hz single-phase AC supply feeds two inductive loads connected in parallel:

- Load 1: Draws 18 A at a power factor of 0.65 lagging
- Load 2: Consumes 1345 W at a power factor of 0.8 lagging
- a) Calculate the apparent power (S1), real power (P1), and reactive power (Q1) for Load-1.
- **b**) Calculate the apparent power (S2), reactive power (Q2), and the current drawn by Load-2.
- c) Determine the total real power (P\_total), total reactive power (Q\_total), and total apparent power (S\_total) of the system before compensation.
- **d**) A capacitor is added in parallel to the combined load to improve the overall power factor to 0.98 lagging. Calculate the reactive power (Qc) that must be supplied by the capacitor.
- e) Determine the required capacitance value (C) in microfarads (µF) for the compensating capacitor.
- f) Calculate the total current drawn from the source after power factor correction.
- Q3. A 600 V (rms), 50 Hz single-phase AC supply feeds two different loads connected in parallel:
  - Load 1: Draws 15 kW at a power factor of 0.9 lagging
  - Load 2: Draws 25 kW at a power factor of 0.95 leading
- a) Calculate the apparent power, reactive power, and current for each load.
- **b**) Determine the total real power (P\_total), total reactive power (Q\_total), and total apparent power (S\_total) of the system before compensation.
- c) Calculate the overall power factor of the system before compensation. State whether it is lagging, leading, or unity.
- d) An inductor is connected in parallel with the system to reduce the power factor to 0.85 lagging (i.e., to intentionally add inductive reactive power). Calculate the inductive reactive power (Q\_L) that must be added.
- e) Determine the required inductance (L) in millihenrys (mH) for the inductor that provides this compensation.
- f) Calculate the new total current drawn from the supply after compensation.

**Q4.** A 440 V (rms), 60 Hz single-phase AC supply feeds three loads connected in parallel:

- Load 1: Draws 15000 W at a power factor of 0.70 lagging
- Load 2: Draws 10000 W at a power factor of 0.95 leading
- Load 3: A passive impedance load given as  $Z=20+j15 \Omega$ .
- a) For Load 1, calculate apparent power, complex power, and reactive power.
- **b**) Repeat part (a) for Load 2.
- c) Repeat part (a) for Load 3.
- **d**) Calculate the current drawn by the impedance.
- e) Calculate the supply current.
- **f**) Determine the total real power, total reactive power, and total apparent power of the entire system (3 loads) before any compensation.
- g) Calculate the overall power factor of the system before compensation. State whether it is lagging, leading, or unity.
- h) What must be done to make the power factor be UNITY. Design a compensation system. Use either a capacitor or an inductor connected parallel to the loads.
- i) Calculate the required amount of reactive power (inductive or capacitive).
- **j**) Determine the total current drawn from the supply after compensation.

**Q5.** A three-phase, 400 V (line-to-line), 50 Hz power supply feeds a large induction motor. The motor delivers 100 hp of mechanical output power and operates at a power factor of 0.75 lagging with an efficiency of 92%. (1 hp = 746 W).

- a) Calculate the input real power (in kW) drawn by the motor from the supply.
- $\label{eq:bound} b) \qquad \mbox{Calculate the apparent power} \ (S) \ \mbox{and reactive power} \ (Q) \ \mbox{consumed by the motor.}$
- c) Determine the line current drawn by the motor from the 400 V three-phase supply.
- **d**) To improve the power factor to 0.95 lagging, a bank of capacitors is connected in parallel with the motor. Calculate the required reactive power (Qc) that must be supplied by the capacitor bank.
- e) Determine the required capacitance per phase (in microfarads, µF) for delta connection of capacitors to supply the required reactive power.
- **f**) Determine the required capacitance per phase (in microfarads, µF) for star connection of capacitors to supply the required reactive power.

**Q6.** A three-phase, 1 kV (line-to-line), 50 Hz supply feeds:

- A large induction motor delivering 400 hp mechanical output power with an efficiency of 93% and operating at a power factor of 0.764 lagging. (1 hp = 746 W).
- An additional balanced resistive load that draws 300 kW of real power
- **a**) Calculate the real input power (in kW) consumed by the motor.
- **b**) Calculate the apparent power (S\_motor) and reactive power (Q\_motor) of the motor.
- c) Determine the total real power (P\_total), total reactive power (Q\_total), and total apparent power (S\_total) of the entire load (motor + resistor).
- d) Calculate the overall power factor of the combined load. Indicate whether it is lagging or leading.
- e) Determine the line current drawn by the combined load from the 400 V, 3-phase supply.
- **f**) Determine the required capacitance per phase (in microfarads, μF) for delta connection of capacitors to raise the power factor to 0.98 lagging.

**Q7.** A 460 V (line-to-line), 50 Hz, three-phase balanced supply feeds the following three loads:

- Load 1 (*Induction Motor*): Delivers 250 hp of mechanical power at 0.75 lagging power factor and 92% efficiency. (1 hp = 746 W).
- Load 2 (*Resistive Load*): Draws 30 kW of real power

• Load 3 (Capacitive Load): A power electronics-based system draws 15 kVAR of leading reactive power

All three loads are connected in parallel.

- a) Calculate the input real power (P\_motor) consumed by the motor.
- **b**) Calculate the apparent power (S\_motor) and reactive power (Q\_motor) of the motor.
- c) Determine the total real power from all three loads.
- d) Determine the total reactive power by accounting for all loads (pay attention to leading vs. lagging sign conventions).
- e) Calculate the total apparent power and the overall power factor of the system. State whether it is lagging, leading, or unity.
- f) Determine the total line current drawn by the system from the three-phase source.
- **g**) Is additional power factor correction required if the goal is to achieve a power factor of 0.95 lagging? Justify your answer using total reactive power.
  - If yes:
    - Calculate the additional reactive power that must be supplied or absorbed.
    - Determine the required capacitance per phase in µF for a delta-connected capacitor bank.
  - If no:
    - Determine the existing power factor and discuss why compensation is not needed.

Prepared by Prof. Dr. A. Mete VURAL