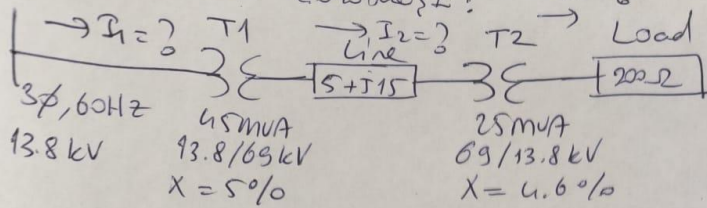


Bu soru deriste cizilmiştir: $I_3 = ?$



$V_{Base, new} = 13.8 \text{ kV}$
 $S_{Base, new} = 80 \text{ MVA}$ } given in the question.
 Primary side of T1.

Solution:


For T1: $Z_{pu, new} = (Z_{pu, old}) \left(\frac{S_{base, new}}{S_{base, old}} \right) \times \left(\frac{V_{base, old}^2}{V_{base, new}^2} \right)$
 $= (j0.05) \times \left(\frac{80 \text{ MVA}}{45 \text{ MVA}} \right) \times \left(\frac{13.8 \text{ kV}}{13.8 \text{ kV}} \right)^2 = \textcircled{A} \text{ pu}$

For Line: $Z_{line, pu} = \frac{Z_{line, actual}}{Z_{Base, line}} = \frac{5 + j15}{\frac{V_{Base, new}^2}{S_{Base, new}}} = \frac{5 + j15}{\frac{(69 \text{ kV})^2}{80 \text{ MVA}}} = \textcircled{B} \text{ pu}$

For T2: $Z_{pu, new} = (j0.046) \left(\frac{80 \text{ MVA}}{25 \text{ MVA}} \right) \left(\frac{69 \text{ kV}}{69 \text{ kV}} \right)^2 = \textcircled{C} \text{ pu}$

For Load: $Z_{Load, pu} = \frac{Z_{Load, actual}}{Z_{Base, load}} = \frac{200}{\frac{(13.8 \text{ kV})^2}{80 \text{ MVA}}} = \textcircled{D} \text{ pu}$

pu impedance diagram is shown below:

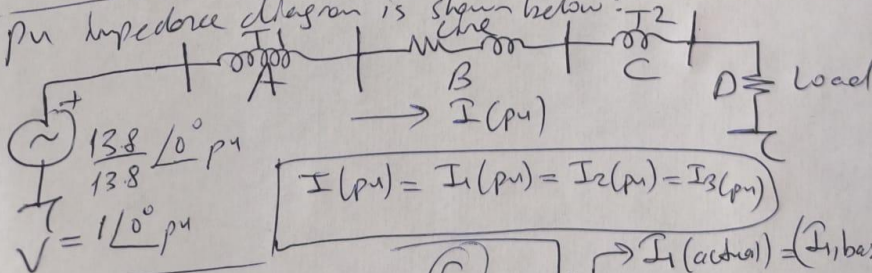

$I_{pu} = \frac{1 \angle 0^\circ}{A + B + C + D} = \textcircled{E} \text{ pu}$

$\rightarrow I_1(\text{actual}) = (I_1, \text{base}) E = \dots$
 $\rightarrow I_2(\text{actual}) = (I_2, \text{base}) E = \dots$
 $\rightarrow I_3(\text{actual}) = (I_3, \text{base}) E = \dots$

In this type of questions, it is important first to define Base values (voltage, power) at each of each transformer.

Source side (or T1 primary)	Line side (or T2 secondary or T1 prim.)
$V_{Base, new} = 13.8 \text{ kV}$	$V_{Base, new} = 69 \text{ kV}$
$V_{Base, old} = 13.8 \text{ kV}$	$V_{Base, old} = 69 \text{ kV}$
$S_{Base, new} = 80 \text{ MVA}$	$S_{Base, new} = 80 \text{ MVA}$
$S_{Base, old} = 45 \text{ MVA (for T1)}$	$S_{Base, old} = 45 \text{ MVA (for T1)}$
	$S_{Base, old} = 25 \text{ MVA (for T2)}$

Load Side:

$$V_{Base, new} = 13.8 \text{ kV}$$

$$V_{Base, old} = 13.8 \text{ kV (due to the T2 sec. rating)}$$

$$S_{Base, new} = 80 \text{ MVA}$$

$$S_{Base, old} = 25 \text{ MVA (if needed)}$$

$$I_{1, base} = \frac{S_{Base, new}}{(\sqrt{3})V_{Base, new}} = \frac{80 \times 10^6}{(\sqrt{3})(13800)} = \text{--- Amps}$$

source side

$$I_{2, base} = \frac{S_{Base, new}}{(\sqrt{3})V_{Base, new}} = \frac{80 \times 10^6}{(\sqrt{3})(69000)} = \text{--- Amps}$$

line side

$$I_{3, base} = \frac{S_{Base, new}}{(\sqrt{3})V_{Base, new}} = \frac{80 \times 10^6}{(\sqrt{3})(13800)} = \text{--- Amps}$$