

Single-Phase Power Calculations: 100 Practice Problems

P (Real), Q (Reactive), S (Complex), $|S|$ (Apparent), and pf (Power Factor)

100 Questions on Single-Phase Power

1. A load has $V = 120$ Vrms and $I = 5$ Arms with a phase difference of 0 degrees. Calculate Real Power P .

Ans: 600 W

2. Calculate the Reactive Power Q for the load in Q1.

Ans: 0 VAR

3. Calculate the Apparent Power $|S|$ for the load in Q1.

Ans: 600 VA

4. What is the Power Factor of a purely resistive load?

Ans: 1.0 (Unity)

5. Define the unit for Complex Power S .

Ans: Volt-Ampere (VA)

6. A load draws 1000 W and 500 VAR. Calculate the magnitude of Complex Power $|S|$.

Ans: 1118.03 VA

7. Calculate the Power Factor for a load with $P = 800$ W and $Q = 600$ VAR.

Ans: 0.8 lagging

8. If the current leads the voltage, is the reactive power positive or negative by convention?

Ans: Negative

9. A 240Vrms source supplies a load with 10A rms at a 30 degree lagging phase angle. Find P .

Ans: 2078.46 W

10. Find the Reactive Power Q for the load in Q9.

Ans: 1200 VAR

11. Find the Apparent Power $|S|$ for the load in Q9.

Ans: 2400 VA

12. If $P = 1500$ W and $|S| = 2000$ VA, calculate the Power Factor.

Ans: 0.75

13. Calculate the reactive power for a load with $|S| = 500$ VA and $pf = 0.6$ leading.

Ans: -400 VAR

14. A circuit has an impedance $Z = 10 + j5$ Ohms. If $I = 2$ A rms, find Real Power P .

Ans: 40 W

15. Find the Reactive Power Q for the circuit in Q14.

Ans: 20 VAR

16. Find the Complex Power S in rectangular form for Q14.

Ans: 40 + j20 VA

17. If $V = 100 \angle 0$ deg and $I = 2 \angle -45$ deg, calculate P .

Ans: 141.42 W

18. Calculate Q for the values in Q17.

Ans: 141.42 VAR

19. Calculate Complex Power S in polar form for Q17.

Ans: 200 \angle 45 deg VA

20. A load has $pf = 0.9$ lagging. Is it inductive or capacitive?

Single-Phase Power Calculations: 100 Practice Problems

P (Real), Q (Reactive), S (Complex), |S| (Apparent), and pf (Power Factor)

Ans: Inductive

21. A 100 Ohm resistor is connected to a 120V rms source. Find P.

Ans: 144 W

22. Find the Apparent Power |S| for the resistor in Q21.

Ans: 144 VA

23. An inductor with reactance $X_L = 50$ Ohms is connected to 100V rms. Find Q.

Ans: 200 VAR

24. Find the Real Power P for the inductor in Q23.

Ans: 0 W

25. A capacitor with reactance $X_C = 40$ Ohms is connected to 120V rms. Find Q.

Ans: -360 VAR

26. Find the Power Factor of a purely capacitive load.

Ans: 0 (leading)

27. If $Z = 30 - j40$ Ohms and $V = 200$ V rms, find |S|.

Ans: 800 VA

28. Find the Real Power P for Q27.

Ans: 480 W

29. Find the Reactive Power Q for Q27.

Ans: -640 VAR

30. Find the Power Factor for the load in Q27.

Ans: 0.6 leading

31. If $I = 5 \angle 30^\circ$ and $Z = 20 \angle -20^\circ$, find S.

Ans: 500 \angle -20 deg VA

32. From Q31, extract P.

Ans: 469.85 W

33. From Q31, extract Q.

Ans: -171.01 VAR

34. A motor draws 5 kVA at 0.85 pf lagging. Find P.

Ans: 4.25 kW

35. Find the Reactive Power Q for the motor in Q34.

Ans: 2.63 kVAR

36. $V(t) = 170 \cos(\omega t)$ and $i(t) = 10 \cos(\omega t - 60)$. Find P.

Ans: 425 W (using RMS: 120.2V * 7.07A * cos 60)

37. Find |S| for the signals in Q36.

Ans: 850 VA

38. Find the pf for the signals in Q36.

Ans: 0.5 lagging

39. A 120V source supplies a 1.2 kW heater. Find current I rms.

Ans: 10 A

40. Find the impedance Z of the heater in Q39.

Ans: 12 Ohms

Single-Phase Power Calculations: 100 Practice Problems

P (Real), Q (Reactive), S (Complex), $|S|$ (Apparent), and pf (Power Factor)

41. Calculate S if $V = 120 \angle 0$ and $I = 10 \angle 30$.

Ans: $1200 \angle -30 \text{ deg VA}$

42. Is the load in Q41 leading or lagging?

Ans: Leading

43. Find P for Q41.

Ans: 1039.23 W

44. Find Q for Q41.

Ans: -600 VAR

45. If $S = 400 + j300 \text{ VA}$, find the pf .

Ans: 0.8 lagging

46. Find the phase angle of the current relative to voltage for Q45.

Ans: -36.87 degrees

47. If $S = 200 - j150 \text{ VA}$, find $|S|$.

Ans: 250 VA

48. Find the pf for Q47.

Ans: 0.8 leading

49. $Z = 4 + j3 \text{ Ohms}$. Source $V = 10 \angle 0 \text{ Vrms}$. Find S .

Ans: $16 + j12 \text{ VA}$

50. What is the apparent power for Q49?

Ans: 20 VA

Single-Phase Power Calculations: 100 Practice Problems

P (Real), Q (Reactive), S (Complex), $|S|$ (Apparent), and pf (Power Factor)

100 Questions on Single-Phase Power (Continued)

51. A load has $P = 500\text{W}$ and $pf = 0.707$ lagging. Find Q .

Ans: 500 VAR

52. Find $|S|$ for Q51.

Ans: 707.11 VA

53. A load has $Q = -1000\text{ VAR}$ and $pf = 0.8$ leading. Find P .

Ans: 1333.33 W

54. Find $|S|$ for Q53.

Ans: 1666.67 VA

55. An impedance $Z = 15 \angle 45^\circ$ Ohms is connected to 240V rms. Find S .

Ans: 3840 \angle 45 deg VA

56. Calculate P for Q55.

Ans: 2715.29 W

57. Calculate Q for Q55.

Ans: 2715.29 VAR

58. If $V = 230 \angle 10^\circ$ and $I = 2 \angle 40^\circ$, find S .

Ans: 460 \angle -30 deg VA

59. Find pf for Q58.

Ans: 0.866 leading

60. Is Q58 inductive or capacitive?

Ans: Capacitive

61. Two loads in parallel: $L_1=100\text{W}$, $L_2=200\text{W}$. Find total P .

Ans: 300 W

62. $L_1=50\text{ VAR}$, $L_2=50\text{ VAR}$. Find total Q .

Ans: 100 VAR

63. $L_1=100\text{W}$, 50VAR ; $L_2=200\text{W}$, -20VAR . Find total S in rectangular form.

Ans: 300 + j30 VA

64. Calculate the total magnitude $|S|$ for Q63.

Ans: 301.49 VA

65. Calculate the total pf for Q63.

Ans: 0.995 lagging

66. Load A: 2kVA at 0.8 pf lag. Find P_a and Q_a .

Ans: $P_a=1.6\text{kW}$, $Q_a=1.2\text{kVAR}$

67. Load B: 1kVA at 0.9 pf lead. Find P_b and Q_b .

Ans: $P_b=0.9\text{kW}$, $Q_b=-0.436\text{kVAR}$

68. Find total P for Load A + Load B in parallel.

Ans: 2.5 kW

69. Find total Q for Load A + Load B in parallel.

Ans: 0.764 kVAR

70. Find total $|S|$ for Load A + Load B in parallel.

Single-Phase Power Calculations: 100 Practice Problems

P (Real), Q (Reactive), S (Complex), |S| (Apparent), and pf (Power Factor)

Ans: 2.614 kVA

71. Find total pf for Load A + Load B in parallel.

Ans: 0.956 lagging

72. A 10 Ohm resistor and 10 Ohm inductive reactance are in parallel. $V = 100V$. Find total P.

Ans: 1000 W

73. Find total Q for Q72.

Ans: 1000 VAR

74. Find total |S| for Q72.

Ans: 1414.21 VA

75. Find the total pf for Q72.

Ans: 0.707 lagging

76. Three loads: $P_1=1kW$, $P_2=2kW$, $P_3=1.5kW$. Total P?

Ans: 4.5 kW

77. $Q_1=1kVAR$, $Q_2=0kVAR$, $Q_3=-0.5kVAR$. Total Q?

Ans: 0.5 kVAR

78. Find total |S| for Q76 & Q77.

Ans: 4.527 kVA

79. Find total pf for Q76 & Q77.

Ans: 0.994 lagging

80. Is the combined load in Q79 leading or lagging?

Ans: Lagging

81. A load at 120V draws 600W at 0.6 pf lag. Find current I rms.

Ans: 8.33 A

82. Find the complex impedance Z for Q81.

Ans: $8.64 + j11.52$ Ohms

83. A device is rated 1200 VA, 120V. Find max current.

Ans: 10 A

84. If the device in Q83 operates at 0.8 pf, find P.

Ans: 960 W

85. Find Q for Q84.

Ans: 720 VAR

86. A transmission line has resistance 0.5 Ohms. A load draws 20A. Find line power loss.

Ans: 200 W

87. Does line loss depend on the load's pf?

Ans: Indirectly, as lower pf requires more current for same P

88. Define Reactive Power in terms of V, I, and theta.

Ans: $Q = V * I * \sin(\theta)$

89. $S = 1000 \angle 0$ deg VA. What is the pf?

Ans: 1.0

90. What is the reactive power for Q89?

Ans: 0 VAR

Single-Phase Power Calculations: 100 Practice Problems

P (Real), Q (Reactive), S (Complex), $|S|$ (Apparent), and pf (Power Factor)

91. A load has $S = j500$ VA. What is the pf ?

Ans: 0

92. Is the load in Q91 purely inductive or purely capacitive?

Ans: Purely inductive

93. A load has $S = -j200$ VA. What is the pf ?

Ans: 0

94. Is the load in Q93 purely inductive or purely capacitive?

Ans: Purely capacitive

95. Calculate S if $V = 100 + j50$ V and $I = 2 - j1$ A.

Ans: $150 + j200$ VA ($S = VI^*$)

96. From Q95, find P .

Ans: 150 W

97. From Q95, find Q .

Ans: 200 VAR

98. From Q95, find $|S|$.

Ans: 250 VA

99. From Q95, find pf .

Ans: 0.6 lagging

100. A load draws 400W and has a phase angle of -30 degrees. Find $|S|$.

Ans: 461.88 VA