

AC Steady-State Sinusoidal Analysis

Study Tutorial with Solutions

Part I: Sinusoidal Waveform Fundamentals

Identify and compute basic properties of sinusoidal signals: amplitude, frequency, period, phase angle, and angular frequency.

1. A voltage is given by $v(t) = 120 \cos(377t + 30^\circ)$ V. Find the amplitude, angular frequency, frequency, period, and phase angle.

Answer: Amplitude $V_m = 120$ V; $\omega = 377$ rad/s; $f = \omega/2\pi = 60$ Hz; $T = 1/f = 16.67$ ms; $\phi = +30^\circ$

2. Write the expression for a sinusoidal current with peak value 5 A, frequency 50 Hz, and phase angle -45° .

Answer: $i(t) = 5 \cos(100\pi t - 45^\circ)$ A [or equivalently $5 \cos(314.16t - 45^\circ)$ A]

3. Convert $v(t) = 10 \sin(1000t + 60^\circ)$ V to cosine form.

Answer: $v(t) = 10 \cos(1000t + 60^\circ - 90^\circ) = 10 \cos(1000t - 30^\circ)$ V

4. Find the RMS value of $v(t) = 170 \cos(377t)$ V.

Answer: $V_{rms} = V_m/\sqrt{2} = 170/\sqrt{2} \approx 120.2$ V

5. Two voltages are $v_1 = 4 \cos(\omega t + 30^\circ)$ and $v_2 = 6 \cos(\omega t - 15^\circ)$. Which leads and by how much?

Answer: v_1 leads v_2 by $30^\circ - (-15^\circ) = 45^\circ$

6. A current $i(t) = 8 \cos(2\pi \cdot 400t - 25^\circ)$ mA. Find its frequency, period, and RMS value.

Answer: $f = 400$ Hz; $T = 2.5$ ms; $I_{rms} = 8/\sqrt{2} \approx 5.66$ mA

7. Convert $i(t) = -6 \cos(\omega t + 40^\circ)$ to a positive cosine expression.

Answer: $i(t) = 6 \cos(\omega t + 40^\circ + 180^\circ) = 6 \cos(\omega t + 220^\circ)$ [or $6 \cos(\omega t - 140^\circ)$] A

8. A 60 Hz sinusoidal voltage has a peak-to-peak value of 340 V. Write its time-domain expression (zero phase).

Answer: $V_{pp} = 340$ V $\rightarrow V_m = 170$ V; $v(t) = 170 \cos(120\pi t)$ V

9. What is the phase difference between $v_1 = 10 \cos(\omega t)$ and $v_2 = 10 \sin(\omega t)$? Which leads?

Answer: $\sin(\omega t) = \cos(\omega t - 90^\circ)$, so v_1 leads v_2 by 90°

10. Find the average power delivered by $v(t) = 170 \cos(377t)$ V across a 10Ω purely resistive load.

Answer: $P = V_{rms}^2/R = (170/\sqrt{2})^2/10 = 14450/10 = 1445$ W

Part II: Phasors — Representation and Conversion

Convert between time-domain sinusoids and phasors. Perform phasor addition, subtraction, and represent signals in polar and rectangular form.

11. Convert $v(t) = 50 \cos(\omega t + 25^\circ)$ V to phasor form.

Answer: $V = 50 \angle 25^\circ$ V (or in rectangular: $50\cos 25^\circ + j50\sin 25^\circ = 45.32 + j21.13$ V)

12. Convert the phasor $I = 3 \angle -40^\circ$ A to time-domain at $\omega = 1000$ rad/s.

Answer: $i(t) = 3 \cos(1000t - 40^\circ)$ A

13. Add the phasors $V_1 = 10 \angle 30^\circ$ V and $V_2 = 8 \angle -45^\circ$ V. Express result in polar form.

Answer: $V_1 = 8.66 + j5$; $V_2 = 5.66 - j5.66$; Sum = $14.32 - j0.66 = 14.33 \angle -2.64^\circ$ V

14. Subtract phasors: $V = V_1 - V_2$ where $V_1 = 6 \angle 60^\circ$ and $V_2 = 4 \angle 30^\circ$. Give in rectangular and polar form.

Answer: $V_1 = 3 + j5.196$; $V_2 = 3.464 + j2$; $V = -0.464 + j3.196 = 3.23 \angle 98.24^\circ$ V

15. Express $I = (3 + j4)$ A in polar form and then as a time-domain current at $\omega = 500$ rad/s.

Answer: $I = 5 \angle 53.13^\circ$ A; $i(t) = 5 \cos(500t + 53.13^\circ)$ A

16. Find the sum $i = i_1 + i_2$ where $i_1 = 4 \cos(\omega t + 30^\circ)$ and $i_2 = 3 \cos(\omega t - 60^\circ)$ using phasors.
Answer: $I_1 = 4\angle 30^\circ$; $I_2 = 3\angle -60^\circ$; $I = 3.464 + j2 + 1.5 - j2.598 = 4.964 - j0.598 = 5\angle -6.87^\circ$ A; $i = 5 \cos(\omega t - 6.87^\circ)$ A
17. Convert $V = 12\angle 150^\circ$ V to rectangular form.
Answer: $V = 12\cos 150^\circ + j12\sin 150^\circ = -10.39 + j6$ V
18. Multiply phasors: $Z_1 = 4\angle 30^\circ$ and $Z_2 = 2\angle 45^\circ$.
Answer: $Z = Z_1 \cdot Z_2 = (4 \times 2)\angle (30^\circ + 45^\circ) = 8\angle 75^\circ$
19. Divide phasors: $V = 20\angle 60^\circ$ V, $I = 4\angle 15^\circ$ A. Find $Z = V/I$.
Answer: $Z = (20/4)\angle (60^\circ - 15^\circ) = 5\angle 45^\circ \Omega$
20. Three phasors: $I_1 = 5\angle 0^\circ$, $I_2 = 3\angle 90^\circ$, $I_3 = 4\angle -90^\circ$. Find $I_{\text{total}} = I_1 + I_2 + I_3$.
Answer: $I = 5 + j3 - j4 = 5 - j1 = 5.1\angle -11.31^\circ$ A

Part III: Impedance of R, L, and C Elements

Compute the impedance of resistors, inductors, and capacitors at given frequencies.

21. Find the impedance of a 47 Ω resistor.
Answer: $Z_R = 47\angle 0^\circ \Omega = 47 + j0 \Omega$ (purely real, no phase shift)
22. Find the impedance of a 10 mH inductor at $f = 60$ Hz.
Answer: $X_L = \omega L = 2\pi(60)(0.01) = 3.77 \Omega$; $Z_L = j3.77 = 3.77\angle 90^\circ \Omega$
23. Find the impedance of a 100 μF capacitor at $\omega = 1000$ rad/s.
Answer: $X_C = 1/(\omega C) = 1/(1000 \times 100 \times 10^{-6}) = 10 \Omega$; $Z_C = -j10 = 10\angle -90^\circ \Omega$
24. At what frequency does a 50 mH inductor have an impedance of magnitude 100 Ω ?
Answer: $X_L = \omega L = 100$; $\omega = 100/0.05 = 2000$ rad/s; $f = 2000/2\pi \approx 318.3$ Hz
25. At what frequency does a 10 μF capacitor have an impedance magnitude of 50 Ω ?
Answer: $X_C = 1/(\omega C) = 50$; $\omega = 1/(50 \times 10 \times 10^{-6}) = 2000$ rad/s; $f \approx 318.3$ Hz
26. Find the impedance of a series R-L circuit with $R = 30 \Omega$ and $L = 40$ mH at $\omega = 500$ rad/s.
Answer: $Z = R + j\omega L = 30 + j(500 \times 0.04) = 30 + j20 = 36.06\angle 33.69^\circ \Omega$
27. Find the impedance of a series R-C circuit with $R = 6 \Omega$ and $C = 200 \mu\text{F}$ at $f = 50$ Hz.
Answer: $X_C = 1/(2\pi \times 50 \times 200 \times 10^{-6}) = 15.92 \Omega$; $Z = 6 - j15.92 = 17.02\angle -69.35^\circ \Omega$
28. Find the total impedance of a series R-L-C circuit: $R = 10 \Omega$, $L = 30$ mH, $C = 100 \mu\text{F}$ at $\omega = 1000$ rad/s.
Answer: $X_L = 30 \Omega$; $X_C = 10 \Omega$; $Z = 10 + j(30 - 10) = 10 + j20 = 22.36\angle 63.43^\circ \Omega$
29. A capacitor $C = 50 \mu\text{F}$ is in parallel with $R = 200 \Omega$ at $\omega = 400$ rad/s. Find Z_{parallel} .
Answer: $Z_C = -j/(\omega C) = -j50 \Omega$; $Z = (200 \times (-j50))/(200 - j50) = -j10000/(200 - j50)$; $|\text{denom}|^2 = 42500$; $Z = 11.76 - j47.06 = 48.51\angle -76^\circ \Omega$
30. Find impedance of parallel R-L combination: $R = 8 \Omega$, $X_L = 6 \Omega$.
Answer: $Z_L = j6$; $Z = (8 \times j6)/(8 + j6) = j48/(8 + j6)$; multiply by conj: $Z = (48 \times 6 + j48 \times 8)/100 = (288 + j384)/100 = 2.88 + j3.84 = 4.8\angle 53.13^\circ \Omega$

Part IV: Ohm's Law and KVL/KCL in Phasor Domain

Apply Ohm's Law $V = IZ$, Kirchhoff's Voltage Law, and Kirchhoff's Current Law in the phasor (frequency) domain.

31. A current $I = 2\angle 30^\circ$ A flows through $Z = 5\angle 45^\circ \Omega$. Find the voltage V .
Answer: $V = IZ = (2 \times 5)\angle (30^\circ + 45^\circ) = 10\angle 75^\circ$ V
32. $V = 120\angle 0^\circ$ V is applied across $Z = 40 + j30 \Omega$. Find the current I .

Answer: $|Z| = \sqrt{(40^2+30^2)} = 50 \Omega$; $\angle Z = \arctan(30/40) = 36.87^\circ$; $I = V/Z = 120/50\angle-36.87^\circ = 2.4\angle-36.87^\circ$ A

33. Apply KVL: $V_s = 100\angle 0^\circ$ V in a series circuit with $V_R = 60\angle 0^\circ$ V and V_L . Find V_L .

Answer: $V_L = V_s - V_R = 100 - 60 = 40\angle 0^\circ$ V... If V_R is purely real and V_L is 90° ahead: $V_L = 100\angle 0^\circ - 60\angle 0^\circ = 40 + j0$ V $\rightarrow 40\angle 0^\circ$ V (or solve with actual impedances if given)

34. A series R-L-C circuit has $V_R = 30\angle 0^\circ$, $V_L = 60\angle 90^\circ$, $V_C = 20\angle -90^\circ$ V. Find total source voltage V_s .

Answer: $V_s = 30 + j60 - j20 = 30 + j40 = 50\angle 53.13^\circ$ V

35. Apply KCL at a node: $I_s = 5\angle 0^\circ$ A, $I_1 = 3\angle 30^\circ$ A. Find $I_2 = I_s - I_1$.

Answer: $I_1 = 2.598 + j1.5$; $I_2 = 5 - 2.598 - j1.5 = 2.402 - j1.5 = 2.836\angle -32^\circ$ A

36. Two impedances $Z_1 = 3 + j4 \Omega$ and $Z_2 = 5 - j2 \Omega$ are in series. A voltage $V = 100\angle 0^\circ$ V is applied. Find I .

Answer: $Z_{total} = 8 + j2 = 8.246\angle 14.04^\circ \Omega$; $I = 100/8.246\angle -14.04^\circ = 12.13\angle -14.04^\circ$ A

37. For the same circuit above, find V_{Z1} and V_{Z2} .

Answer: $V_{Z1} = I \cdot Z_1 = 12.13\angle -14.04^\circ \times 5\angle 53.13^\circ = 60.65\angle 39.09^\circ$ V; $V_{Z2} = 12.13\angle -14.04^\circ \times 5.385\angle -21.8^\circ = 65.31\angle -35.84^\circ$ V

38. Three impedances in parallel: $Z_1 = 10\angle 0^\circ$, $Z_2 = 5\angle 90^\circ$, $Z_3 = 20\angle -90^\circ \Omega$; source $50\angle 0^\circ$ V. Find total current.

Answer: $I_1 = 5\angle 0^\circ$, $I_2 = 10\angle -90^\circ$, $I_3 = 2.5\angle 90^\circ$; $I_T = 5 - j10 + j2.5 = 5 - j7.5 = 9.01\angle -56.31^\circ$ A

39. $V_s = 50\angle 30^\circ$ V drives a circuit with $Z = 10\angle -60^\circ \Omega$. Write $i(t)$ at $\omega = 377$ rad/s.

Answer: $I = 50/10\angle(30^\circ - (-60^\circ)) = 5\angle 90^\circ$ A; $i(t) = 5 \cos(377t + 90^\circ)$ A

40. In a parallel R-L circuit, $R = 4 \Omega$, $X_L = 3 \Omega$, $V = 12\angle 0^\circ$ V. Find I_R , I_L , and I_{total} .

Answer: $I_R = 12/4\angle 0^\circ = 3\angle 0^\circ$ A; $I_L = 12/3\angle -90^\circ = 4\angle -90^\circ$ A; $I_T = 3 - j4 = 5\angle -53.13^\circ$ A

Part V: Nodal and Mesh Analysis in AC Circuits

Apply nodal voltage and mesh current methods to AC circuits in phasor domain.

41. A simple two-node circuit: node 1 connected to source $I_s = 2\angle 0^\circ$ A, shunt $Z_1 = j5 \Omega$ to ground, and $Z_2 = 10 \Omega$ to ground. Find V_1 .

Answer: $Y = 1/Z_1 + 1/Z_2 = 1/(j5) + 1/10 = 0.1 - j0.2$; $V_1 = I_s/Y = 2/(0.1 - j0.2) = 2(0.1 + j0.2)/0.05 = 4 + j8 = 8.944\angle 63.43^\circ$ V

42. Write the nodal equation for a circuit with two nodes (V_1 , V_2) and admittances $Y_{11} = 0.5$, $Y_{12} = -0.2$, $Y_{22} = 0.4$ S with $I_{s1} = 3$ A and $I_{s2} = 1$ A.

Answer: $0.5V_1 - 0.2V_2 = 3$ and $-0.2V_1 + 0.4V_2 = 1$; Solving: $V_1 = 7.5$ V, $V_2 = 6.25$ V

43. Mesh analysis: single mesh with $V_s = 50\angle 0^\circ$ V, $R = 6 \Omega$, $X_L = 8 \Omega$ in series. Find mesh current I .

Answer: $Z = 6 + j8 = 10\angle 53.13^\circ \Omega$; $I = 50/10\angle -53.13^\circ = 5\angle -53.13^\circ$ A

44. Two-mesh circuit: Mesh 1 has $V_s = 100\angle 0^\circ$, $Z_1 = 10\Omega$, $Z_{12} = j5\Omega$ (mutual). Mesh 2 has $Z_2 = 8\Omega$, same Z_{12} . Set up mesh equations.

Answer: $(10+j5)I_1 - j5I_2 = 100$ and $-j5I_1 + (8+j5)I_2 = 0$; These are the two mesh equations (solve with Cramer's rule or substitution)

45. Using superposition, find V_x due to two sources: $V_{s1} = 10\angle 0^\circ$ V (alone gives $V_{x'} = 4\angle 30^\circ$ V) and $V_{s2} = 6\angle 90^\circ$ V (alone gives $V_{x''} = 2\angle 45^\circ$ V). Find total V_x .

Answer: $V_x = V_{x'} + V_{x''} = 4\angle 30^\circ + 2\angle 45^\circ = 3.464 + j2 + 1.414 + j1.414 = 4.878 + j3.414 = 5.93\angle 34.96^\circ$ V

46. Find the Thevenin equivalent of a circuit seen from terminals AB: $V_{oc} = 40\angle 30^\circ$ V and $Z_{th} = 3 + j4 \Omega$.

Answer: $V_{th} = 40\angle 30^\circ$ V; $Z_{th} = 3 + j4 = 5\angle 53.13^\circ \Omega$. These fully define the Thevenin equivalent.

47. A load $Z_L = 4 - j3 \Omega$ is connected to a Thevenin source $V_{th} = 20\angle 0^\circ \text{ V}$, $Z_{th} = 4 + j3 \Omega$. Find I_L .
Answer: $Z_{total} = (4+j3)+(4-j3) = 8 \Omega$; $I_L = 20/8\angle 0^\circ = 2.5\angle 0^\circ \text{ A}$
48. For maximum power transfer in AC, what must Z_L equal given $Z_{th} = 5 + j8 \Omega$?
Answer: For maximum average power: $Z_L = Z_{th}^* = 5 - j8 \Omega$ (complex conjugate of source impedance)
49. Find Norton equivalent: $I_{sc} = 4\angle -20^\circ \text{ A}$, $Z_N = 10\angle 60^\circ \Omega$.
Answer: $I_N = 4\angle -20^\circ \text{ A}$; $Z_N = 10\angle 60^\circ \Omega$. The Norton equivalent is a current source $4\angle -20^\circ \text{ A}$ in parallel with $10\angle 60^\circ \Omega$.
50. Convert Thevenin ($V_{th} = 50\angle 45^\circ \text{ V}$, $Z_{th} = 5\angle 30^\circ \Omega$) to Norton equivalent.
Answer: $I_N = V_{th}/Z_{th} = 50/5\angle(45^\circ - 30^\circ) = 10\angle 15^\circ \text{ A}$; $Z_N = Z_{th} = 5\angle 30^\circ \Omega$

Part VI: AC Power — Real, Reactive, and Apparent

Calculate real power P (W), reactive power Q (VAR), apparent power S (VA), power factor, and complex power $S = P + jQ$.

51. A load draws $I = 5\angle -36.87^\circ \text{ A}$ from $V = 100\angle 0^\circ \text{ V}$. Find P , Q , S , and power factor.
Answer: $\theta = 0^\circ - (-36.87^\circ) = 36.87^\circ$; $P = V_{rms}I_{rms}\cos\theta = 100 \times 5 \times \cos 36.87^\circ = 400 \text{ W}$; $Q = 100 \times 5 \times \sin 36.87^\circ = 300 \text{ VAR}$ (inductive); $S = 500 \text{ VA}$; $\text{pf} = \cos 36.87^\circ = 0.8$ lagging
52. Compute complex power $S = V \cdot I^*$ where $V = 120\angle 30^\circ \text{ V}$ and $I = 4\angle -15^\circ \text{ A}$ (rms values).
Answer: $I^* = 4\angle +15^\circ$; $S = 120 \times 4\angle(30^\circ + 15^\circ) = 480\angle 45^\circ \text{ VA} = 339.4 + j339.4 \text{ VA}$; $P = 339.4 \text{ W}$, $Q = 339.4 \text{ VAR}$
53. A resistor $R = 25 \Omega$ carries $I_{rms} = 4 \text{ A}$. Find P , Q , and S .
Answer: $P = I^2R = 16 \times 25 = 400 \text{ W}$; $Q = 0 \text{ VAR}$ (resistor); $S = 400 \text{ VA}$; $\text{pf} = 1.0$
54. A pure inductor $X_L = 10 \Omega$ has $I_{rms} = 3 \text{ A}$. Find P , Q , and S .
Answer: $P = 0 \text{ W}$; $Q = I^2X_L = 9 \times 10 = 90 \text{ VAR}$ (inductive/positive); $S = 90 \text{ VA}$; $\text{pf} = 0$ lagging
55. A pure capacitor $X_C = 8 \Omega$ has $I_{rms} = 2 \text{ A}$. Find P , Q , and S .
Answer: $P = 0 \text{ W}$; $Q = -I^2X_C = -32 \text{ VAR}$ (capacitive/negative); $S = 32 \text{ VA}$; $\text{pf} = 0$ leading
56. A load $Z = 6 + j8 \Omega$ is connected to $V_{rms} = 100\angle 0^\circ \text{ V}$. Find P , Q , and power factor.
Answer: $I = 100/10\angle -53.13^\circ = 10\angle -53.13^\circ \text{ A}$; $P = I^2R = 100 \times 6 = 600 \text{ W}$; $Q = I^2X = 100 \times 8 = 800 \text{ VAR}$; $\text{pf} = \cos 53.13^\circ = 0.6$ lagging
57. Two loads in parallel: Load 1: $P_1 = 500 \text{ W}$, $\text{pf}_1 = 0.8$ lag; Load 2: $P_2 = 300 \text{ W}$, $\text{pf}_2 = 1.0$. Find total P , Q , S .
Answer: $Q_1 = P_1 \times \tan(\cos^{-1}0.8) = 500 \times 0.75 = 375 \text{ VAR}$; $Q_2 = 0$; $P_T = 800 \text{ W}$; $Q_T = 375 \text{ VAR}$; $S_T = \sqrt{(800^2 + 375^2)} = 880.8 \text{ VA}$
58. A factory load: $S = 10 \text{ kVA}$ at $\text{pf} = 0.6$ lagging from 240 V rms . Find P , Q , and line current.
Answer: $P = S \times \text{pf} = 6000 \text{ W}$; $Q = S \times \sin(\cos^{-1}0.6) = 8000 \text{ VAR}$; $I = S/V = 10000/240 = 41.67 \text{ A}$
60. Three loads on a 120 V rms source: Load A: 200 W at $\text{pf}=1$; Load B: 150 W at $\text{pf}=0.5$ lag; Load C: 100 VAR capacitive. Find total S .
Answer: $Q_B = 150 \times \tan(\cos^{-1}0.5) = 259.8 \text{ VAR}$; $Q_C = -100 \text{ VAR}$; $S_T = (200+150) + j(0+259.8-100) = 350 + j159.8 = 384.8\angle 24.6^\circ \text{ VA}$