

EXPERIMENT 7 LC FILTERS 2

Frequency characteristics of Bandpass and Bandreject Filters

PRELIMINARY WORK

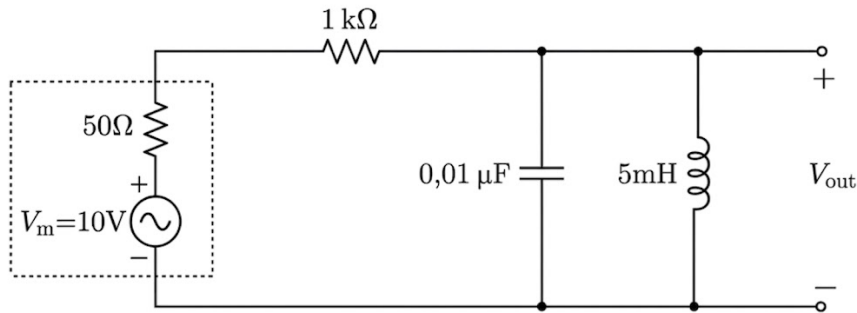


Figure 1

P1 For the filter given in Figure 1,

- a) Obtain the transfer function $V_o(\omega)/V_i(\omega)$.
- b) Identify the type of filter.
- c) Compute the center frequency, ω_0 .
- d) Calculate the cutoff frequencies, ω_1 and ω_2 , the bandwidth, β , and the quality factor Q .

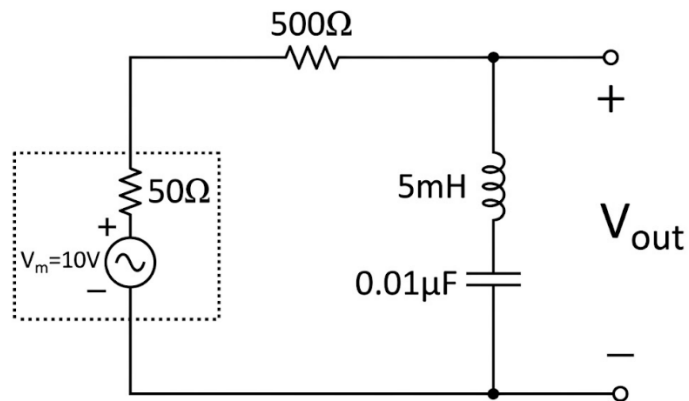


Figure 2

P2 For the filter given in Figure 2,

- a) Obtain the transfer function $V_o(\omega)/V_i(\omega)$.
- b) Identify the type of filter.
- c) Compute the center frequency, ω_0 .
- d) Calculate the cutoff frequencies, ω_1 and ω_2 , the bandwidth, β , and the quality factor Q .

EXPERIMENTAL WORK

E1 Bandpass Filter Analysis

1. Construct the parallel RLC circuit shown in Figure 1.
2. Set the Function Generator to provide a sine wave with a peak voltage of $V_m = 10V$.
Connect the generator to the circuit input (V_i).
3. Connect **Channel 1** of the oscilloscope across the input source.
Connect **Channel 2** across the parallel LC combination to measure V_{out} .
4. Vary the frequency from 1 kHz to 100 kHz.
 - a. Locate the Center Frequency f_0 where V_{out} reaches its maximum value.
 - b. Find the Cutoff Frequencies (f_1 and f_2) where the output voltage drops to 0.707 of the maximum value ($V_{out_max}/\sqrt{2}$).

E2 Bandreject (Notch) Filter Analysis

1. Reconfigure the components to match the series LC structure shown in Figure 2.
2. Maintain the input at $V_m = 10V$.
3. Connect Channel 2 of the oscilloscope to measure V_{out} across the series LC branch.
4. Vary the frequency from 1 kHz to 100 kHz.
 - a. Sweep the frequency to find the Notch Frequency (f_0) where V_{out} is at its minimum (ideally zero).
 - b. Identify the frequencies (f_1 and f_2) where the signal begins to recover to 0.707 of the input level.