

EXPERIMENT 7

LC FILTERS

Frequency characteristics of lowpass and highpass filters

PRELIMINARY WORK

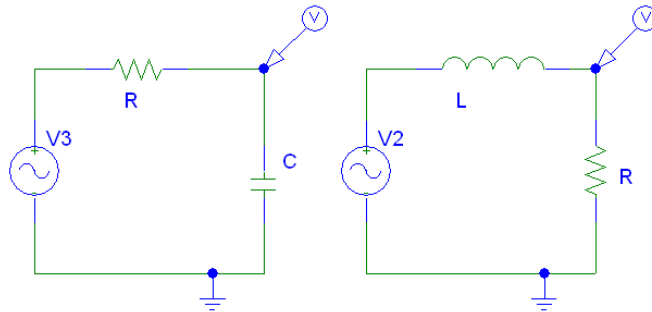


Figure 1

a) Series RC circuit

b) Series RL circuit

P1 For the series circuit in Figure 1 a. Determine the type of filter

- Find the transfer function between the source voltage and the output voltage
- What is the attenuation in dB?
- Determine an equation for the cutoff frequency in the series RC circuit
- Find the value of R that will result in a cutoff frequency of 3183 Hz if capacitor value is chosen as 0.1 μ F

Plot the gain curve in PSPICE by choosing the values as C=0.1 μ F and the resistance value is chosen as the value that you found in P1 d

P2 For the series circuit in Figure 1 b. Determine the type of filter

- Find the transfer function between the source voltage and the output voltage.
- What is the attenuation in dB?
- Determine an equation for the cutoff frequency in the series RL circuit
- Find the value of R that will result in a cutoff frequency of 3183 Hz if Inductor value is chose as 5mH

Plot the gain curve in PSPICE by choosing the values as L=5mH and the resistance value is chosen as the value that you found in P2 d

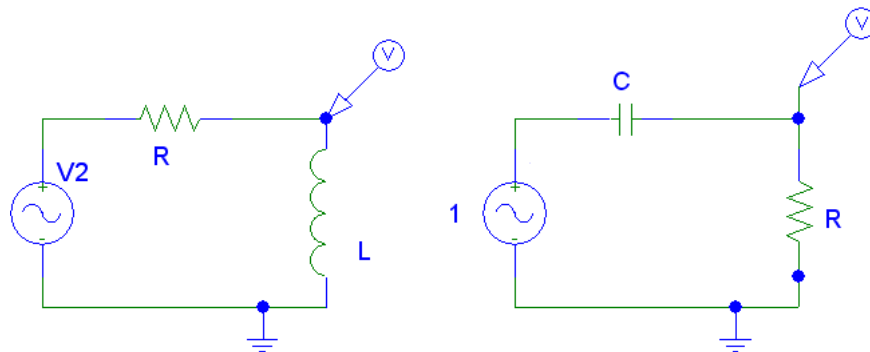


Figure 2

a) Series RL circuit b) Series RC circuit

P3 For the series circuit in Figure 2 a. Determine the type of filter

- Find the transfer function between the source voltage and the output voltage
- What is the attenuation in dB?
- Determine an equation for the cutoff frequency in the series RL circuit
- Find the value of R that will result in a cutoff frequency of 3183 Hz if Inductor value is chosen as 5mH

Plot the gain curve in PSPICE by choosing the values as $L=5\text{mH}$ and the resistance value is chosen as the value that you found in P3 d

P4 For the series circuit in Figure 2 b. Determine the type of filter

- Find the transfer function between the source voltage and the output voltage
- What is the attenuation in dB?
- Determine an equation for the cutoff frequency in the series RC circuit
- Find the value of R that will result in a cutoff frequency of 3183 Hz if capacitor value is chosen as 0.1 μF

Plot the gain curve in PSPICE by choosing the values as $C=0.1\mu\text{F}$ and the resistance value is chosen as the value that you found in P4 d

EXPERIMENTAL WORK

E1 Setup the circuit given in figure 1 a. By changing the frequency of signal generator, obtain the Voltage transfer function between input and output. Please choose at least 20 proper frequency values up to 20 KHz. **Indicate cutoff frequencies on your plot.**

E2 Repeat E1 for Figure 1 b

E3 Repeat E1 for Figure 2 a

E4 Repeat E1 for Figure 2b